 


1 AND 2's COMPLEMENT:


- 1's: simply invert all bits.
 - $-2^{(n-1)} - 1$ to $+2^{(n-1)} - 1$
- 2's: start on right until first 1: invert remaining bits.
 - $-2^{(n-1)}$ to $+2^{(n-1)} - 1$

CIRCUITS FOR ADDERS AND FAST ADDERS:


- Fast-Adder



Full-Adder

 

Half-Adder

 

SINGLE & DOUBLE PRECISION IEEE FLOATING POINT FORMATS:

- Decimal to float:
 - Convert to binary (abs. value), move to mantissa and keep track of power (<- negative, -> positive), exponent = 127 + power from above, find binary of this #, then place mantissa behind this # and add sign in front of both.
- Fraction to float:
 - Convert to binary (take # * 2, keep track of # before decimal, continue multiplying decimal until decimal = 0). MSB is at the top, LSB at bottom. Opposite of normal.
 - Repeat same steps from above.
- IEEE Float to Decimal:
 - Mark off sign, mark off and find exponent, find value ($2^{(\text{exponent} - 127)}$), find mantissa ($1 + \frac{1}{2} + \frac{1}{4} \dots$ the 1 is always included), multiply by value ($2^{(\text{exponent} - 127)}$), adhere to sign.

MULTIPLEXERS:

- 2^n to 1, n select lines. # of MUX = size of each number. Size of MUX = amount of numbers.

 


Figure 2: Implementation of AND gate using a 2:1 mux

 


Figure 6: Implementation of 2-input OR gate using 2:1 mux

 


Figure 14: Implementation of NOT gate using 2x1 mux

SHANNON'S EXPANSION:


- Always start by pulling out MSB after writing entire function.
- $F = \sim \text{MSB}() + \text{MSB}()$
- Continue until contents are single value.
 - Values pulled out are select line values.
 - Single values within are data inputs.

DECODERS:


- n to 2^n

En	w_1	w_0	y_0	y_1	y_2	y_3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

 


DEMULTIPLEXERS:


- Used to reverse an input to 2^n outputs:
 - 1-4 deMUX can make 2-4 decoder.
 - 1-8 deMUX can make 3-8 decoder.

ENCODERS:

- 2^n to n
- Binary ("one-hot" encoded):

 


- Priority:

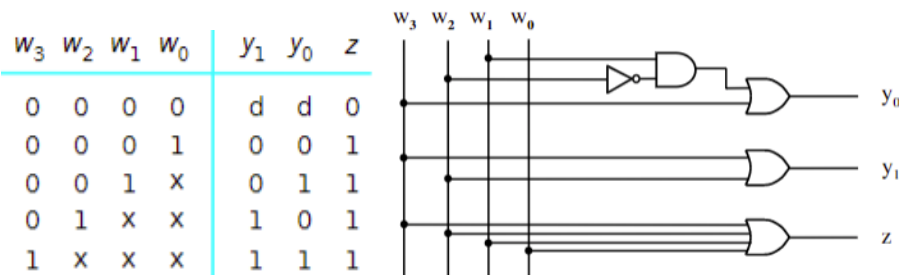

CODE CONVERTERS:

- Shifter:

 

K-MAPS FOR 2, 3, & 4 VARIABLES:

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

x_2	x_1	
0	0	m_0
0	1	m_2
1	0	m_1
1	1	m_3

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

x_3	$x_1 x_2$	00	01	11	10
0		m_0	m_2	m_6	m_4
1		m_1	m_3	m_7	m_5


(b) Karnaugh map

x_1	x_2	x_3	x_4	
0	0	0	0	m_0
0	0	0	1	m_1
0	0	1	0	m_2
0	0	1	1	m_3
0	1	0	0	m_4
0	1	0	1	m_5
0	1	1	0	m_6
0	1	1	1	m_7
1	0	0	0	m_8
1	0	0	1	m_9
1	0	1	0	m_{10}
1	0	1	1	m_{11}
1	1	0	0	m_{12}
1	1	0	1	m_{13}
1	1	1	0	m_{14}
1	1	1	1	m_{15}

$x_3 x_4$	$x_1 x_2$	00	01	11	10
00		m_0	m_4	m_{12}	m_8
01		m_1	m_5	m_{13}	m_9
11		m_3	m_7	m_{15}	m_{11}
10		m_2	m_6	m_{14}	m_{10}

LATCHES (SR, GATED SR, GATED D):

 
- SR w/ NOR (if using NAND, swap and negate R and S, characteristics table gets inverted):




\bar{S}	\bar{R}	Q_s	Q_b
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0/1	1/0 (no change)

S	R	Q_s	Q_b
0	0	0/1	1/0 (no change)
0	1	0	1
1	0	1	0
1	1	1	1


- Gated SR:

 


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

 

- Gated D:

 


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

 


FLIP-FLOPS (D F.F., T F.F., AND JK F.F.):


- D (Positive-edge, Negative-edge):

 

- T (Positive-edge, Negative-edge):

 


- JK (Positive-edge, Negative-edge):

 


REGISTERS & REGISTER FILES:


- Parallel-Access Register:

 

Shift Register:

 

- Parallel-Access-Shift Register:

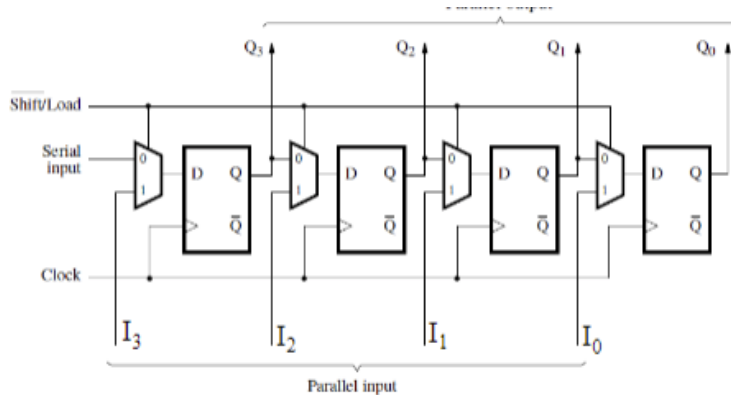

COUNTERS: