

~~Dr. [unclear]~~

04/17/22


Homework 8

1) • Mealy machines - a FSM whose output values are determined by both its current state & current inputs.

• asynchronous

• Moore machines - a FSM whose output values are only determined by its current state.

• synchronous & delayed output

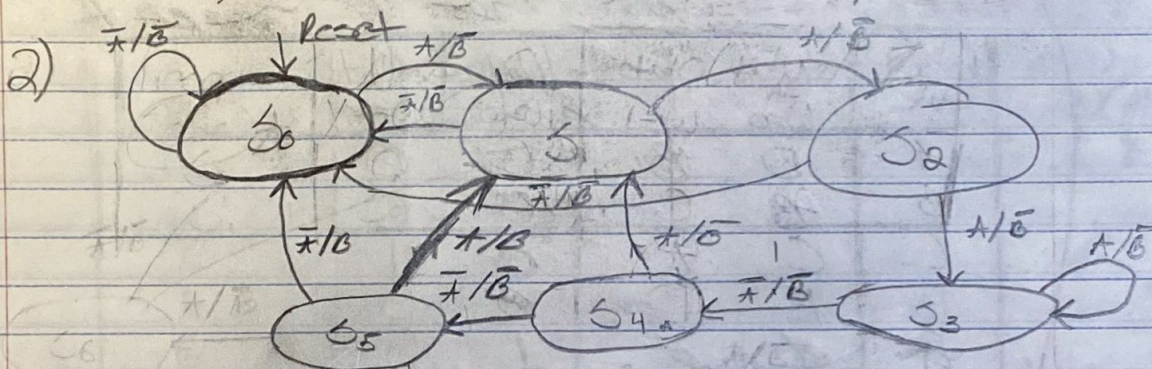


* NOT SURE HOW TO PUT IN STATE DIAGRAM

3)

Present State $v_2 v_1 v_0$	X	Next State $v_2 v_1 v_0$	Output Z
000	0	000	0
000	1	001	0
001	0	010	0
001	1	011	0
010	0	100	1
010	1	101	1
011	0	110	1
011	1	111	1
100	0	000	0
100	1	101	1
101	0	010	0
101	1	100	0
110	0	011	0
110	1	110	0
111	0	011	0
111	1	111	0

- 4) a) • A: 00001
 • B: 00010
 • C: 00100
 • D: 01000
 • E: 10000

b)

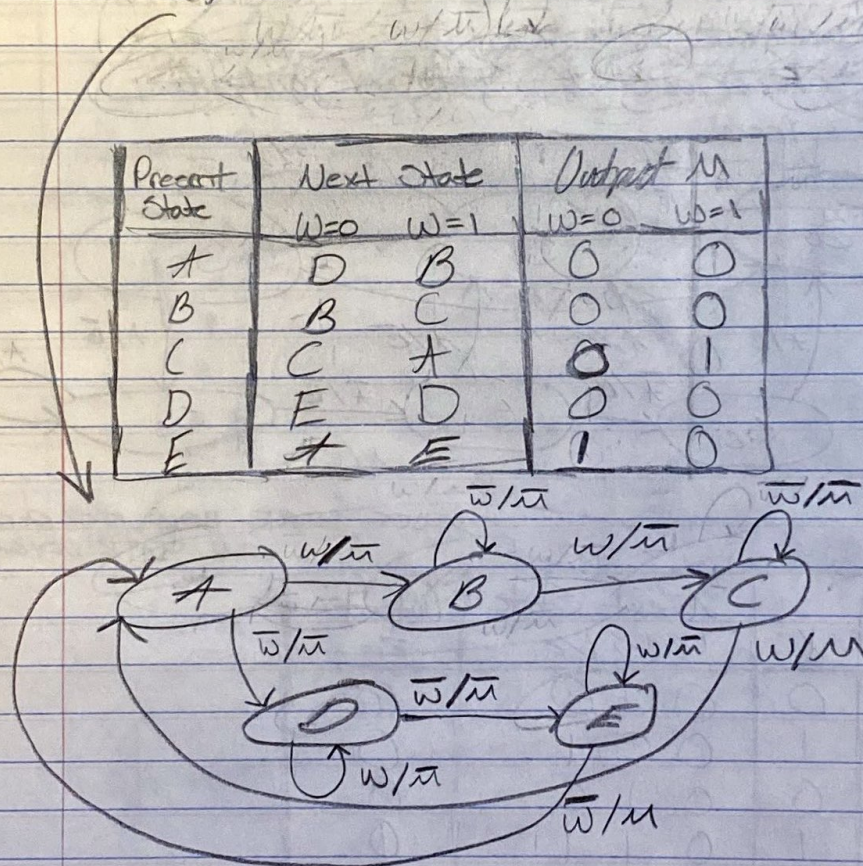

c)

Present state	Next state		Output z	
	w=0 Y	w=1 Y	w=0 Z	w=1 Z
A	01000	00010	0	0
B	00010	00100	0	0
C	00100	00001	0	1
D	01000	10000	0	0
E	10000	00001	1	0


- d)
- $A = \bar{w}A + wA$
 - $B = \bar{w}B + wB$
 - $C = \bar{w}C + wC$
 - $D = \bar{w}D + wD$
 - $E = \bar{w}E + wE$
 - $M = wC + \bar{w}E$

e) The particular circuit has the same # of states as it does state variables because it is one-hot encoded.

5)


Present State	Next State		Output
	w=0	w=1	
A	A	B	0
B	A	C	0
C	D	F	0
D	H	E	0
E	B	H	1
F	G	F	0
G	H	E	0
H	A	B	0

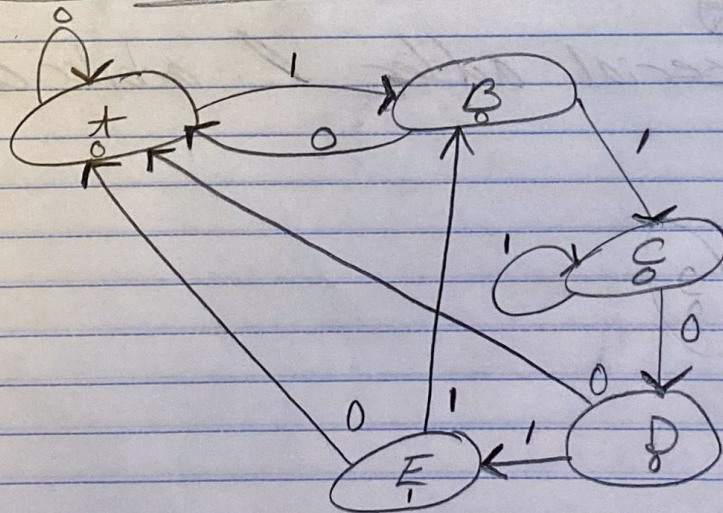$P1: (A B C D E F G H)(E)$
 $P2: (D G)(A B C F H)(E')$
 $P3: (E)(D G)(C F)(A B H)$
 $P4: (E)(D G)(C F)(B)(A H)$




6) a) 8 minimum state variables because of K-successes
 b) 3 T.F.F's are required to implement this FSM

c) 96 transitions

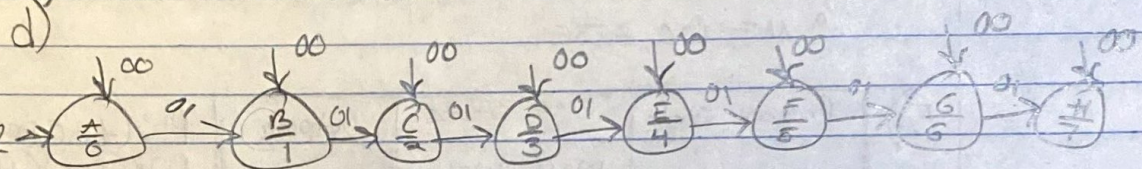

• 24 states & 80 transitions

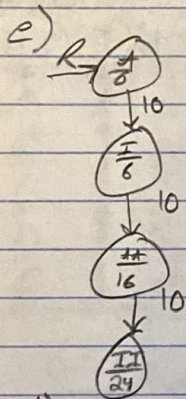

• 28 states & 92 transitions

f) serial adder & arbiter circuit