

Devon Amrdahl

Lab 3 Answer Sheet

Name and Student ID: Devon Amrdahl 053855830 Lab Section: 1

Date: 2/8/22

PRELAB:

Q1. Read section 3.0 and fill in the truth table below for Design 1 (*the farmer's problem*). Then use it to construct the POS expression.

Cabbage	Goat	Wolf	Alarm
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

POS Logic Expression: $(C + \bar{G} + W)(\bar{C} + G + \bar{W})$

TA Initials: _____

Lab 3 Answer Sheet

Q2. Read section 4.0 and fill in the truth table below for Design 2 (*adding the farmer*). Then use it to construct the SOP expressions.

Farmer	Cabbage	Goat	Wolf	Alarm
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0
1	1	1	1	0

$$\begin{aligned} & \overline{F}G\overline{W} + F\overline{G}\overline{W} + F\overline{C}\overline{G}\overline{W} \\ & + \overline{F}C\overline{G}\overline{W} \end{aligned}$$

$$\Rightarrow \overline{FG}(w + c\overline{w}) = \overline{FG}(w + c)$$

$$\checkmark \Rightarrow F\bar{G}(\bar{\omega} + \bar{c} \cdot \omega) \Rightarrow$$

$$F\overline{G}(\overline{w}+\overline{c})$$

$$\Rightarrow \overline{F}G\overline{W} + \overline{F}G\overline{C} + F\overline{G}\overline{W} + F\overline{G}\overline{C}$$

✓✓✓

FC

✓

	00	01	11	10
00	00	01	11/3	10/2
01	01	10/5	11/7	10/6
11	11/4	10/3	11/5	10/1
10	11/8	11/9	11/1	10/0

$$\Rightarrow F\bar{G}\bar{w} + F\bar{C}\bar{b} + \bar{F}Gw + \bar{F}Cb$$

Canonical SOP Logic Expression: $\overline{F}\overline{C}G\overline{W} + \overline{F}\overline{C}G\overline{W} + \overline{F}FG\overline{W} + \overline{F}\overline{C}\overline{G}\overline{W} + \overline{F}\overline{C}G\overline{W} + \overline{F}\overline{C}\overline{G}\overline{W}$

Simplified SOP Logic Expression: $\underline{F\bar{G}\bar{W} + \bar{F}G\bar{W} + F\bar{C}\bar{G} + \bar{F}C\bar{G}}$

TA Initials: _____

LAB:

3.0 Simulation results demonstrate correct code. TA Initials: Schematic (FPGA) *SK*

Schematic (FPGA) Link-5

Structural (ModelSim) M.K.S Behavioral (ModelSim) M.K.S

4.0 Simulation results demonstrate correct code. TA Initials: M. K. S