


Name and Std No.: Danial 053855820 Lab Section: 1

Date: 04/04/22


PRELAB:

Refer to Chapter 5 in your textbook and the lab instructions to complete your pre-lab. Please read all the material and complete the circuit diagrams before you come to the lab.

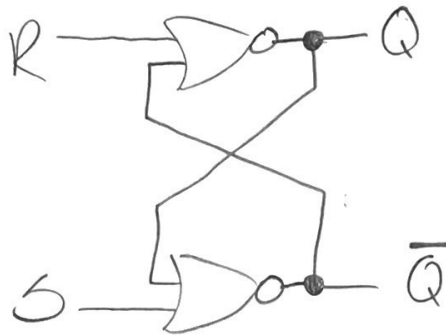
Q1. Draw the circuit diagram for the SR Latch using NOR Gates for **Section 2.0** in the space below.



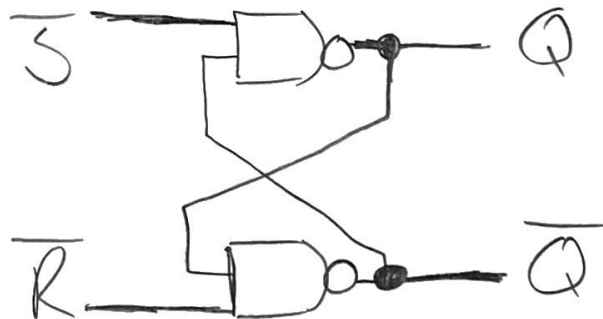
Q2. Draw the circuit diagram for the $\overline{S}\overline{R}$ Latch using NAND Gates for **Section 2.0** in the space below.



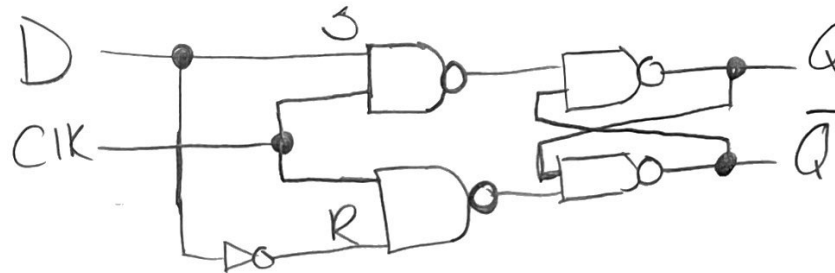
Q3. Draw the circuit diagram for the D Latch using NAND Gates and a NOT gate for Section 3.0 in the space below.



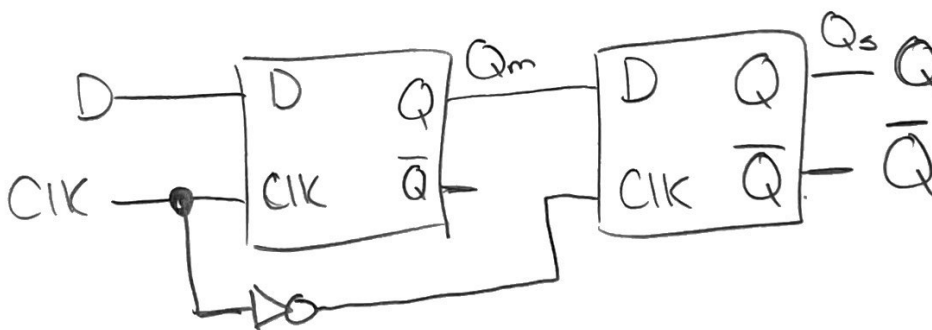Q4. Draw the circuit diagram for the D Flip-Flop for Section 4.0 using the D latches you built in the previous step in the space below. The flip-flop should be triggered by the negative edge of the clock.



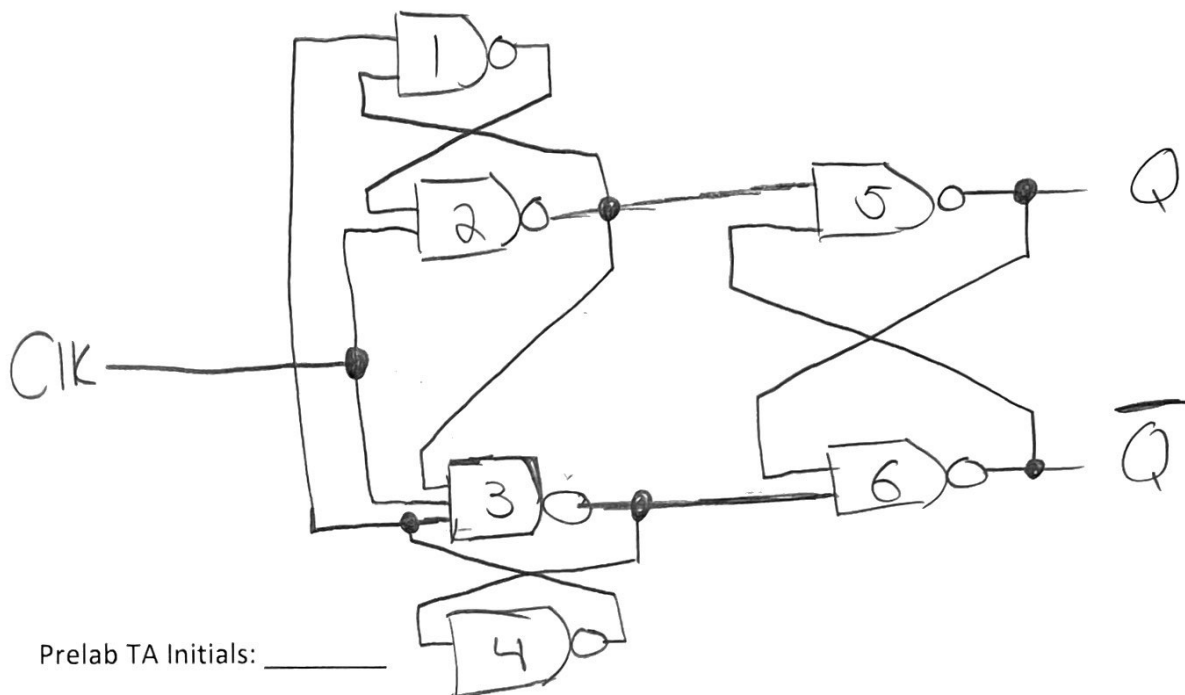Q5. Draw the circuit diagram for the Positive-Edge-Triggered D Flip-Flop using NAND gates for **Section 4.0** in the space below.



LAB:

2.0 Complete the characteristic table for both versions of the SR latch. Do both versions function properly as a latch? YES

SR NOR Latch		
S	R	Action
0	0	Keep State
0	1	$Q = 0$
1	0	$Q = 1$
1	1	Restricted Combination

$\overline{S}\overline{R}$ NAND Latch		
S	R	Action
0	0	Restricted
0	1	$Q = 1$
1	0	$Q = 0$
1	1	Keep State


ModelSim results demonstrate a good circuit. TA Initials: NOR M.16.5 NAND M.16.5

Lab 9 Answer Sheet

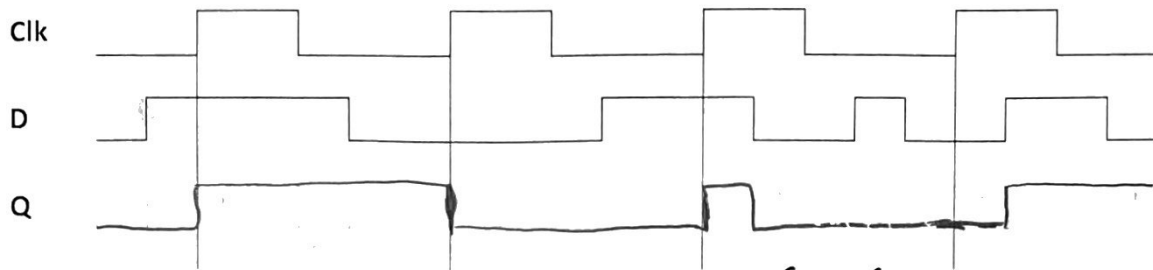3.0 Complete the timing diagram below for your Gated D Latch.


What is the difference between this gated latch and the previous basic latches?

when CLK=1 Q follows D, otherwise keeps value




Hardware results demonstrate a good circuit. TA Initials: M.145

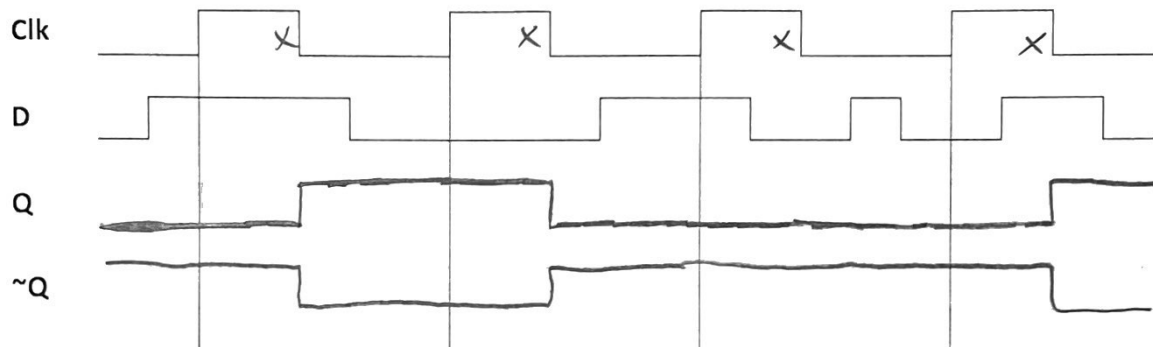4.0 Complete the timing diagram below for your Negative-Edge-Triggered D Flip-Flop.



Hardware results demonstrate a good circuit. TA Initials: M.145

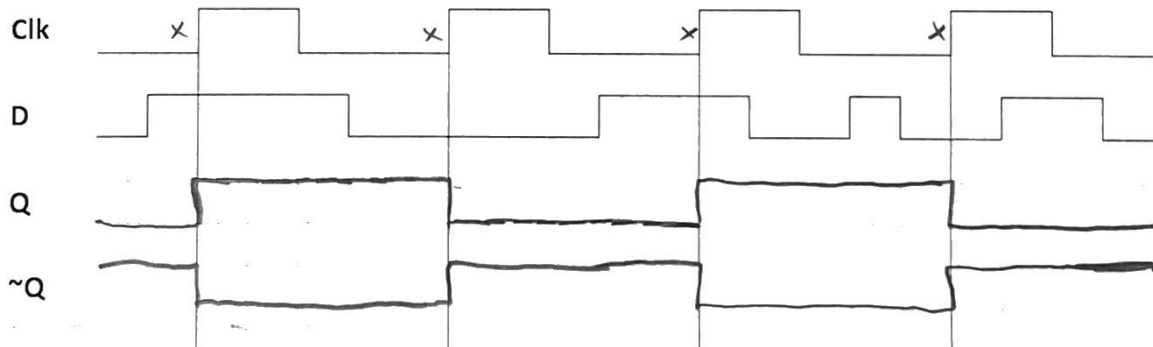Complete the timing diagram below for your Positive-Edge-Triggered D Flip-Flop.



Hardware results demonstrate a good circuit. TA Initials: M.145