


Name and Std No.: David Hall 053855820 Lab Section: 1

Date: 04/04/22


PRELAB:

Refer to Chapter 5 in your textbook and the lab instructions to complete your pre-lab. Please read all the material and complete the circuit diagrams before you come to the lab.

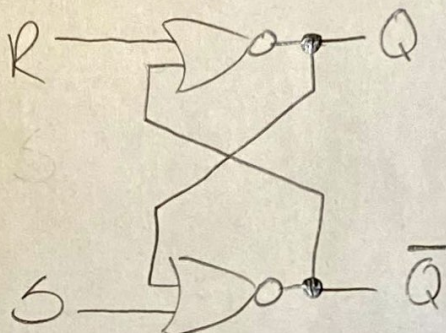
Q1. Draw the circuit diagram for the SR Latch using NOR Gates for Section 2.0 in the space below.



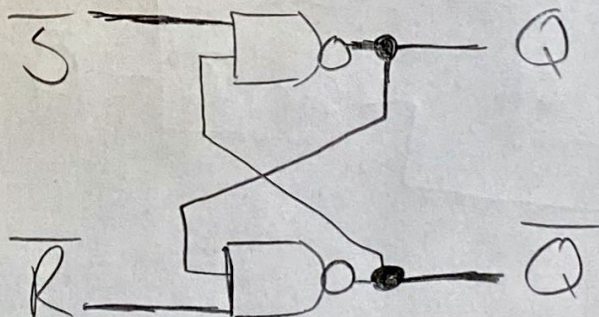
Q2. Draw the circuit diagram for the $\bar{S}\bar{R}$ Latch using NAND Gates for Section 2.0 in the space below.



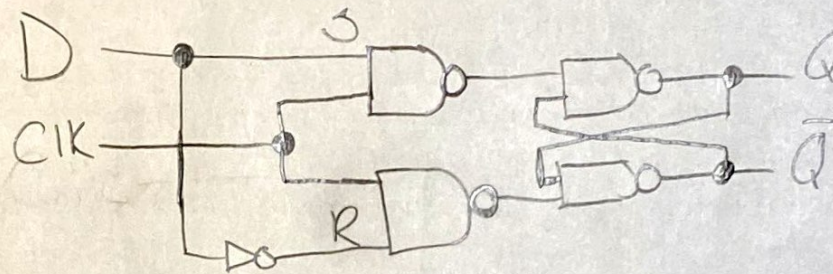
Q3. Draw the circuit diagram for the D Latch using NAND Gates and a NOT gate for **Section 3.0** in the space below.



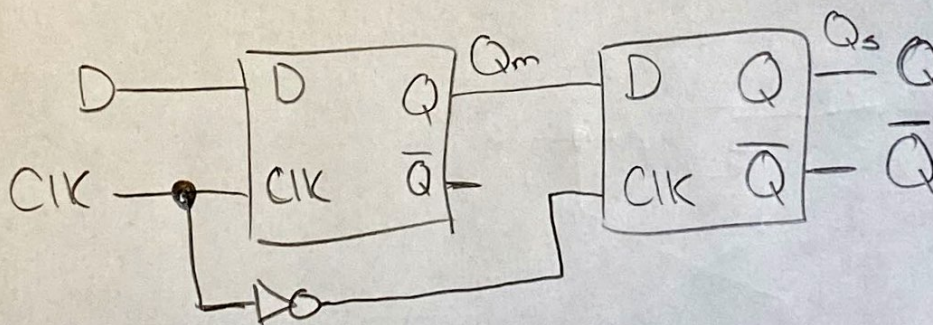Q4. Draw the circuit diagram for the D Flip-Flop for **Section 4.0** using the D latches you built in the previous step in the space below. The flip-flop should be triggered by the negative edge of the clock.



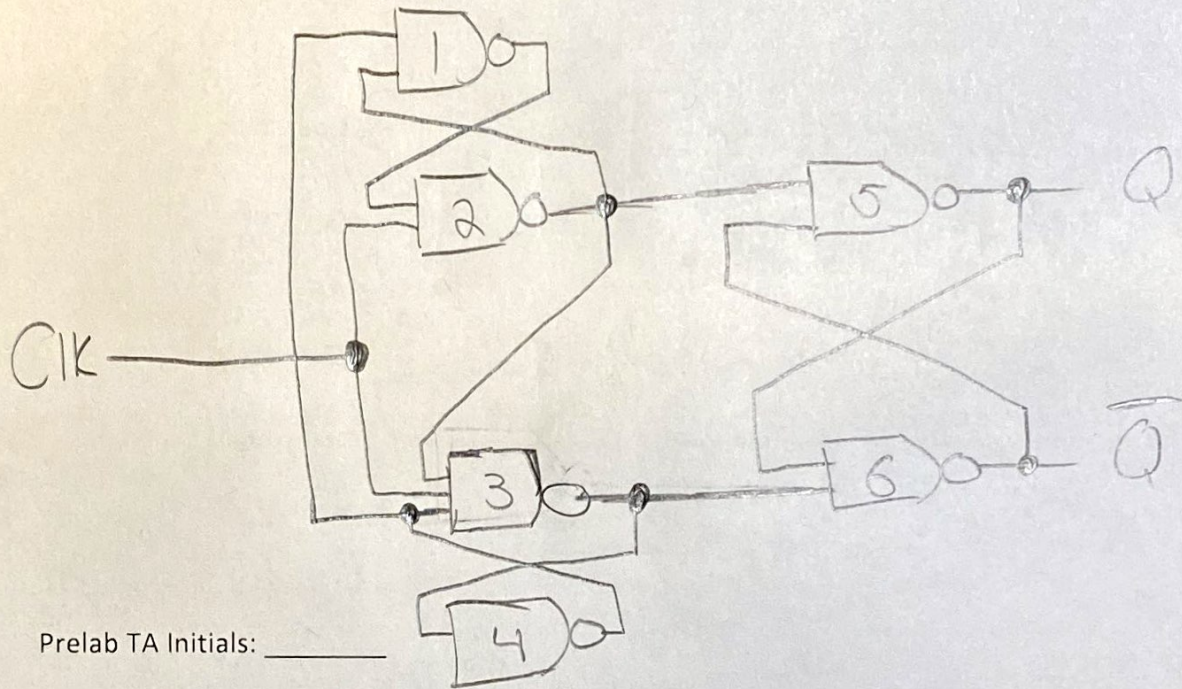Q5. Draw the circuit diagram for the Positive-Edge-Triggered D Flip-Flop using NAND gates for Section 4.0 in the space below.



Prelab TA Initials: _____

LAB:

2.0 Complete the characteristic table for both versions of the SR latch. Do both versions function properly as a latch? _____

SR NOR Latch		
S	R	Action
0	0	Keep State
0	1	$Q =$
1	0	$Q =$
1	1	Restricted Combination


$\overline{S}\overline{R}$ NAND Latch		
S	R	Action
0	0	
0	1	$Q =$
1	0	$Q =$
1	1	

ModelSim results demonstrate a good circuit. TA Initials: NOR _____ NAND _____

Lab 9 Answer Sheet

 
3.0 Complete the timing diagram below for your Gated D Latch.

What is the difference between this gated latch and the previous basic latches?




Hardware results demonstrate a good circuit. TA Initials: _____

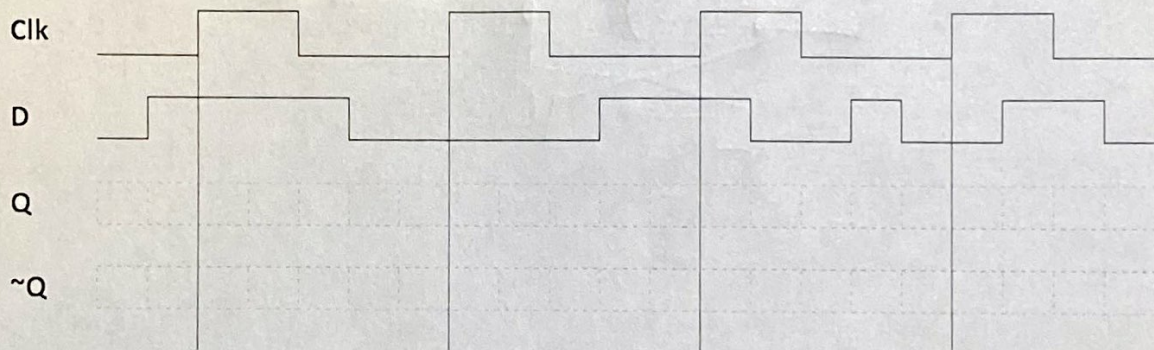4.0 Complete the timing diagram below for your Negative-Edge-Triggered D Flip-Flop.



Hardware results demonstrate a good circuit. TA Initials: _____

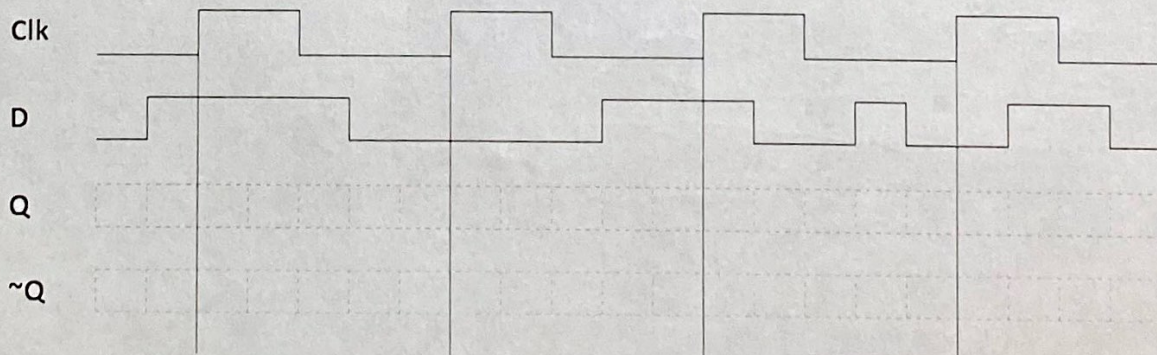Complete the timing diagram below for your Positive-Edge-Triggered D Flip-Flop.



Hardware results demonstrate a good circuit. TA Initials: _____