


Name & Std No.: Amrullah 05351830 Lab Section: 1Date: 04/11/22**PRELAB:**

Refer to Chapter 5 in your textbook and the lab instructions to complete your pre-lab. Please read all the material and complete the circuit diagrams before you come to the lab.

Q1. Draw the circuit diagram for the 4-bit **Shift Register** using D flip-flops in the space below.




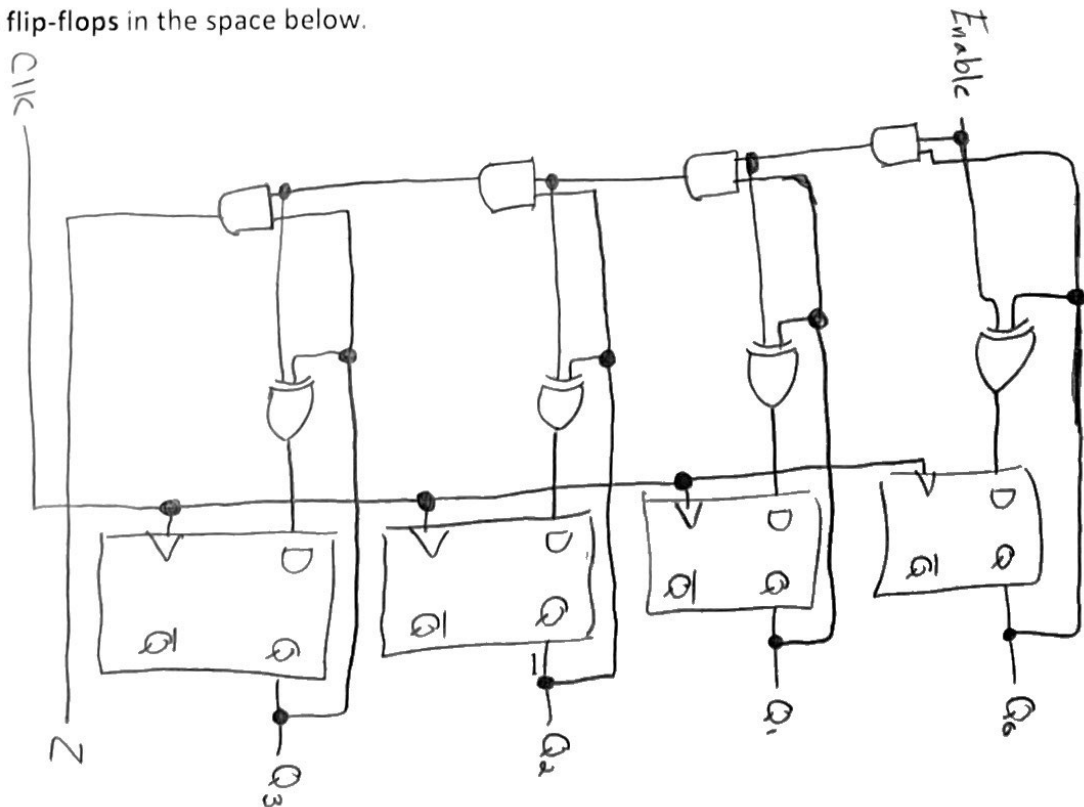Q2. Draw the circuit diagram for the 4-bit **Synchronous Up-Counter with Enable** using D flip-flops in the space below.




*\* shall we include clear as well?*

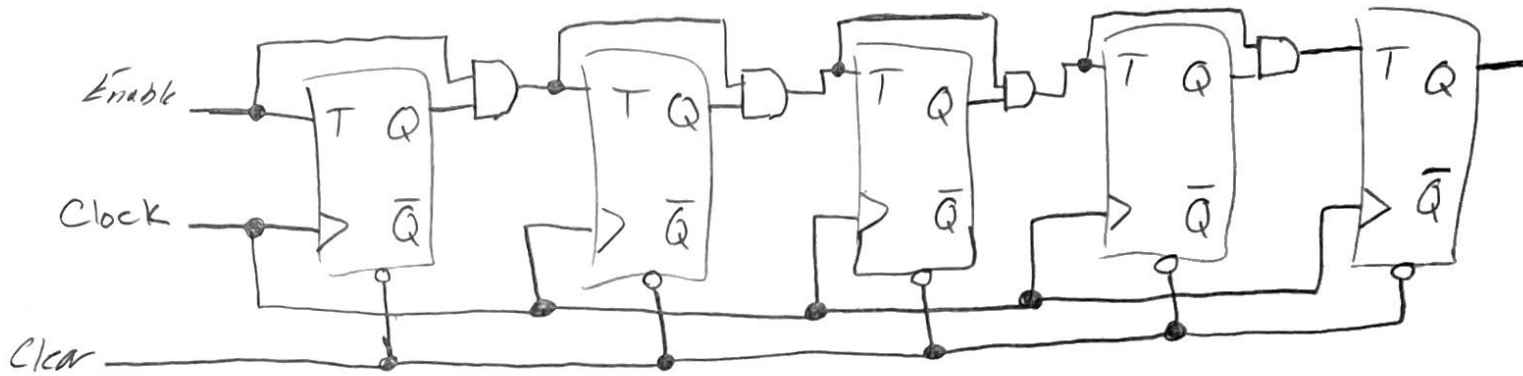
**Q3.** Draw the circuit diagram for a 5-bit Synchronous Up-Counter with Enable using T flip-flops in the space below.



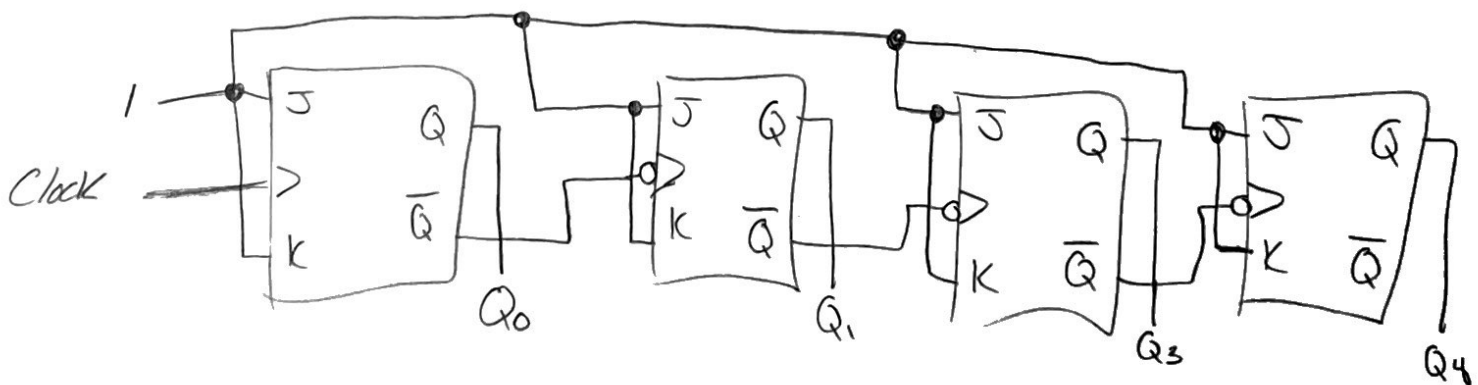**Q4.** Draw the circuit diagram for the 4-bit Asynchronous Up-Counter using JK flip-flops in the space below.



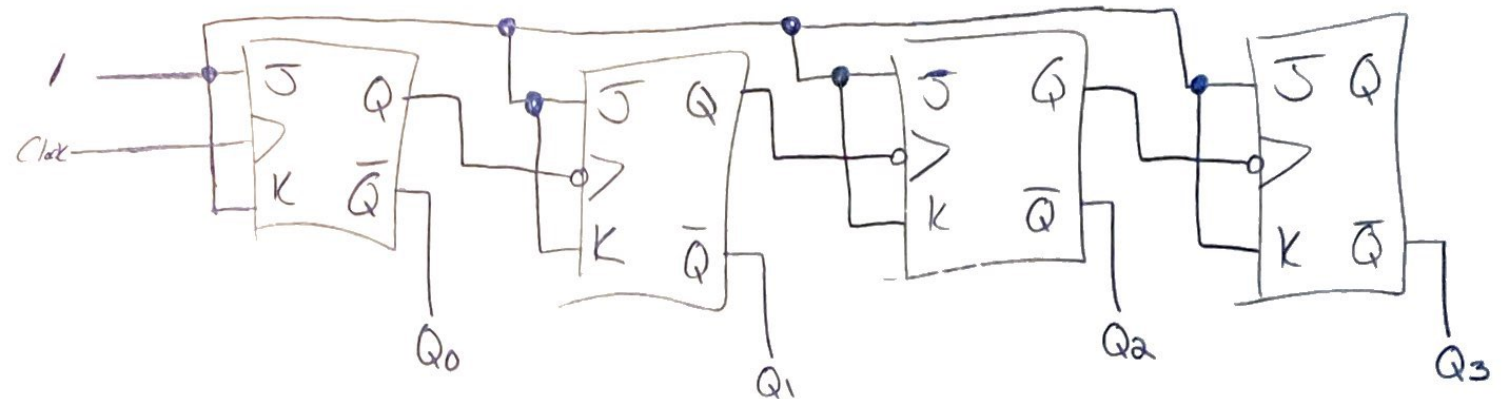Q5. Draw the circuit diagram for the 4-bit **Asynchronous Down-Counter** using JK flip-flops in the space below.



**LAB:**

2.0 Fill in the sequence table below.

| Time  | Q1  | Q2  | Q3  | Q4  | Set IN |
|-------|-----|-----|-----|-----|--------|
| T = 0 | n/a | n/a | n/a | n/a | 1      |
| T = 1 |     | n/a | n/a | n/a | 0      |
| T = 2 |     |     | n/a | n/a | 1      |
| T = 3 |     |     |     | n/a | 1      |
| T = 4 |     |     |     |     | 0      |
| T = 5 |     |     |     |     | 1      |
| T = 6 |     |     |     |     | 1      |
| T = 7 |     |     |     |     | n/a    |

ModelSim results demonstrate a good circuit. TA Initials: \_\_\_\_\_

3.1 ModelSim results demonstrate a good circuit using **DFFs**. TA Initials: \_\_\_\_\_

ModelSim results demonstrate a good circuit using **TFFs**. TA Initials: \_\_\_\_\_

3.2 Seven segment shows 0 to F while counting up. TA Initials: \_\_\_\_\_

Seven-segment display shows F to 0 while counting down. TA Initials: \_\_\_\_\_