

Don't Mind

04/22/22

Quiz 11

1) $0 \rightarrow 5 \rightarrow 7 \rightarrow 1$

• state encoding

A: 000

B: 101


C: 111

D: 001

• will need 3 flip flops because 3 bits

• synchronous

a)

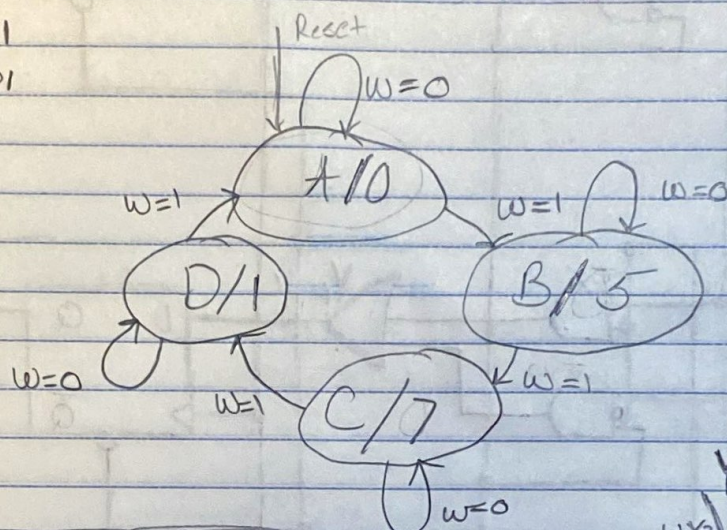

b)

Present State $y_2 y_1 y_0$	Next State		Count
	$w=0$ $y_2 y_1 y_0$	$w=1$ $y_2 y_1 y_0$	
000	000	101	000
101	101	111	101
111	111	001	111
001	001	000	001

y_0	$w y_2$	$x y_0$	01	11	10
00	0	1	d	d	
01	d	1	1	d	
11	d	1	1	d	
10	1	0	d	d	

y_1	$w y_2$	$x y_0$	00	01	11	10
00	0	0	d	d		
01	d	0	1	d		
11	d	1	0	d		
10	0	0	d	d		

$y_2 y_1 y_0$	$w y_2$	00	01	11	10
00	0	0	d	d	
01	d	1	1	d	
11	d	1	0	d	
10	1	0	d	d	


\Rightarrow


$$Y_0 = \bar{w} y_0 + y_2 + w \bar{y}_2 \bar{y}_0$$

$$Y_1 = \bar{w} y_1 + w y_2 \bar{y}_1$$


$$Y_2 = y_2 \bar{y}_1 + \bar{w} y_2 + w \bar{y}_2 \bar{y}_0$$

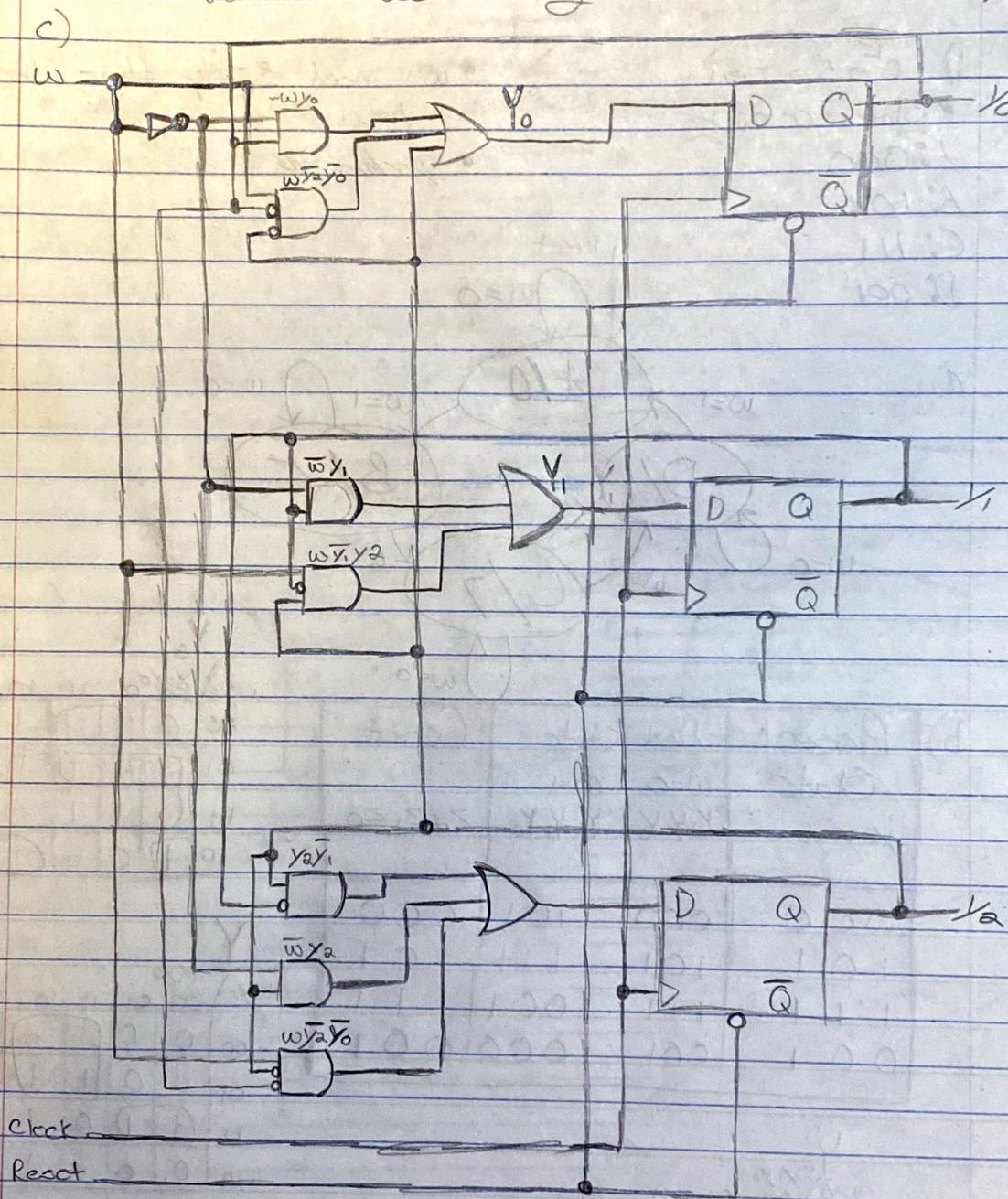* also forgot the XOR simplification pattern
 * should have been using \bar{Q} to make it simpler



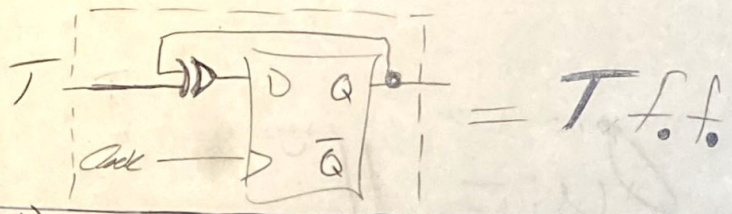

d)

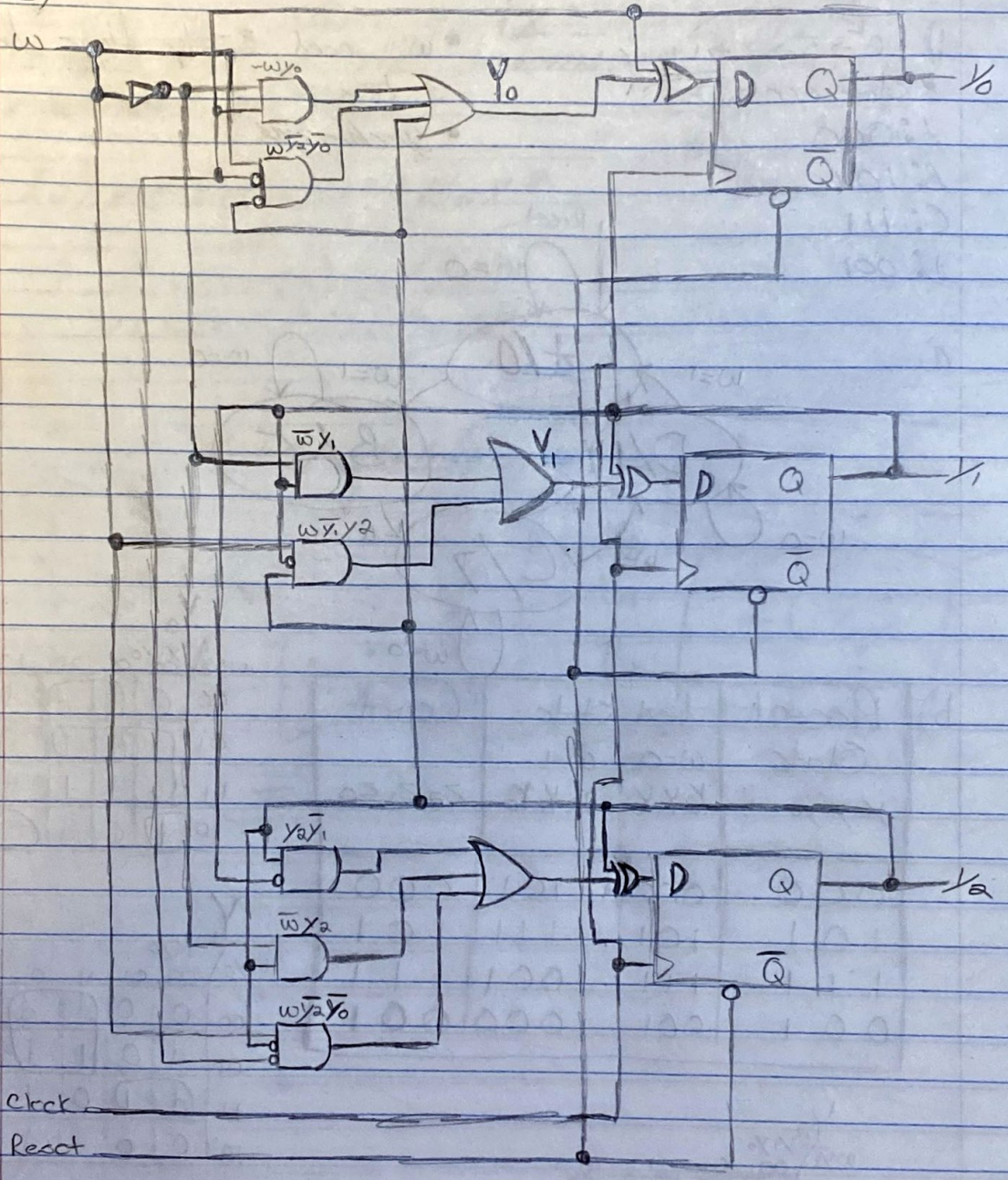

2)

- a)
- $Z = y_1 + y_0$
 - $y_1 = \overline{y_0}$
 - $y_0 = w \oplus y_1$

b)

	Present State $y_1 y_0$	Next State		Output Z
		$w=0$ $y_1 y_0$	$w=1$ $y_1 y_0$	
A	0 0	1 0	1 1	0
B	0 1	0 0	0 1	1
C	1 0	1 1	1 0	1
D	1 1	0 1	0 0	1

c)

