

Dr. Hall (PRE 281) Quiz 2

1) a) $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C$

\Rightarrow 12a. Distributive

$\Rightarrow \overline{A}\overline{B}(\overline{C} + C) + A\overline{B}(\overline{C} + C)$

$\Rightarrow \overline{A}\overline{B}(1) + A\overline{B}(1) \Rightarrow 8b.$

$\Rightarrow \overline{A}\overline{B} + A\overline{B}$

6a.

$\Rightarrow \overline{B}(\overline{A} + A)$

14a. combining

$\Rightarrow \overline{B}$




b) \overline{B}

c) \overline{B}

c) $(A+B+C)(A+\overline{B}+\overline{C})(\overline{A}+\overline{B}+C)(\overline{A}+B+\overline{C})$

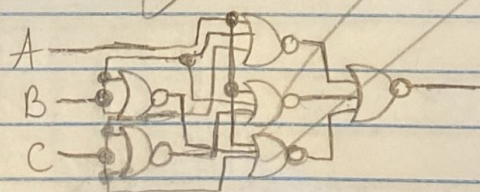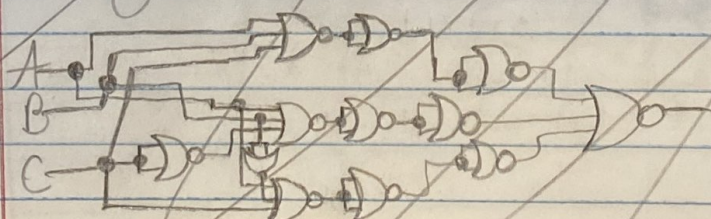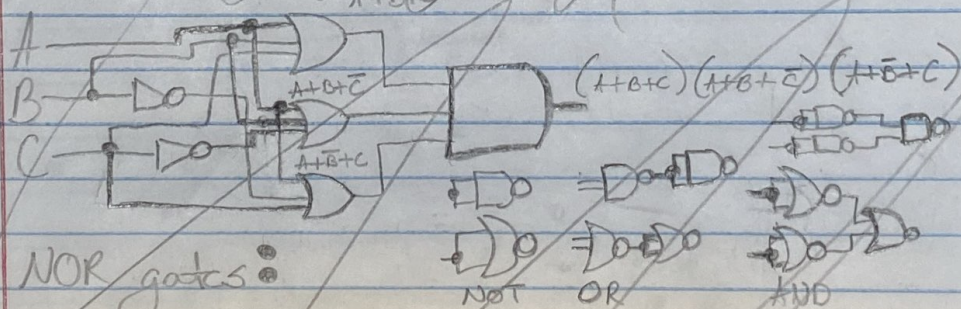2) $f(x_1, x_2, x_3) = \prod M(0, 1, 2)$

$\Rightarrow (A+B+C)(A+\overline{B}+\overline{C})(\overline{A}+\overline{B}+C)$




$$\Rightarrow (X_1 + X_2 + X_3)(X_1 + X_2 + \bar{X}_3)(X_1 + \bar{X}_2 + X_3)$$


$$\hookrightarrow (X_1 + X_2 + X_3)(X_1 + X_2 + \bar{X}_3) \Rightarrow (X_1 + X_2) \quad \text{14b. Combining}$$

$$\Rightarrow (X_1 + X_2)(X_1 + \bar{X}_2 + X_3) \Rightarrow (X_1 + X_2)(X_1 + X_3)$$

$$\Rightarrow (X_1 + X_2)(X_1 + X_3)$$

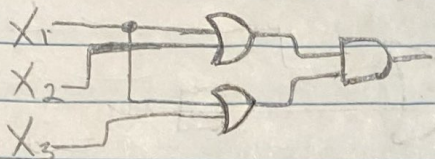

NOW w/ NOR gates: (POS)

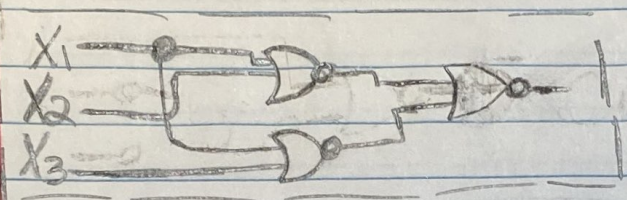

$$3) f(X_1, X_2, X_3) = \prod M(0, 1, 5, 6, 7)$$


$$\Rightarrow \sum m(2, 3, 4)$$

$$\Rightarrow \bar{X}_1 X_2 \bar{X}_3 + \bar{X}_1 X_2 X_3 + X_1 \bar{X}_2 \bar{X}_3 \quad (\text{SOP})$$

$$= \bar{X}_1 X_2 (\bar{X}_3 + X_3) + X_1 \bar{X}_2 \bar{X}_3 \Rightarrow \bar{X}_1 X_2 (1) + X_1 \bar{X}_2 \bar{X}_3$$

$$\Rightarrow \bar{X}_1 X_2 + X_1 \bar{X}_2 \bar{X}_3$$

* Don't know how to simplify further.

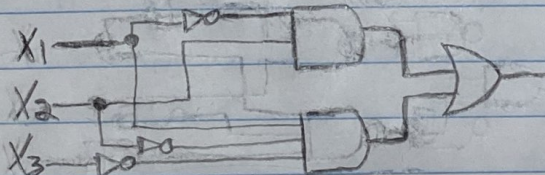

NOW w/ NAND gates:

