

**CprE 281: Digital Logic**  
**Midterm 2: Friday, Oct 23, 2020**

**Student Name:** \_\_\_\_\_

**Student ID:** \_\_\_\_\_

**1. True/False Questions (10 x 1p each = 10p)**

- |   |              |
|---|--------------|
| (a) In a JK flip-flop, when $J=K=0$ , the output $Q(n+1) = Q(n)$ .  | TRUE / FALSE |
| (b) In 2's complement notation, $1101_2 < 1110_2$   | TRUE / FALSE |
| (c) A 1-to-64 MUX requires 6 select lines.  | TRUE / FALSE |
| (d) A 4-to-16 Decoder has one hot encoded output.   | TRUE / FALSE |
| (e) In 2's complement notation: $0011_2 + 1011_2 = 0000_2$  | TRUE / FALSE |
| (f) Any logic function can be implemented with a Decoder and an OR gate.  | TRUE / FALSE |
| (g) A gated D-Latch changes its output only when the clock level is 1.  | TRUE / FALSE |
| (h) In 2's complement notation, a three-bit number can represent any number from <b>-8<sub>10</sub></b> to <b>+8<sub>10</sub></b> . | TRUE / FALSE |
| (i) Any Boolean function can be implemented using only D flip-flops.  | TRUE / FALSE |
| (j) A 1-to-4 Demultiplexer can be built with a 2-to-4 Decoder.  | TRUE / FALSE |

**2. Logic circuits (20p)**

In all sub-problems, draw the complete wiring diagram using logic gates (no-high-level graphical symbols are allowed in this problem). Clearly label all the inputs and outputs.

- (a) (5 points) Gated SR Latch (with NOR gates for the latch)

- (b) (15 points) Implement a four-bit shift register that provides the parallel access. The control signal Shift/Load is used to select the mode of operation. If Shift/Load = 0, then the circuit operates as a shift register. If Shift/Load = 1, then the parallel input data are loaded into the register. In both cases the action takes place on the positive edge of the clock. Label all the inputs and outputs.

### 3. Addition/Subtraction (3x5 = 15p)

Assume the following binary numbers are represented in 6-bit 2's complement form. Perform the following operations. In each case, write the carries generated clearly and indicate whether or not overflow occurs. [Note: For subtraction, first convert it into addition.]

(a)  $110101 + 001111$

(b)  $10111 - 100101$

(c)  $101110 - 110001$

#### 4. Number Conversions (4 x 5p each = 20p)

(a) What is the decimal value of the binary number  $10011_2$  if it is in the following form:

- I. Unsigned binary
- II. Sign-and-magnitude
- III. 1's complement
- IV. 2's complement

(b) Convert the following number to IEEE 754 Single Precision Floating Point format: **-24.0**

(c) Convert the following number to IEEE 754 Single Precision Floating Point format: **0.625**


(d) Convert the following number from IEEE 754 Single Precision Floating Point format to 4-bit 2's complement format:

0011111101100000000000000000


### 5. Timing Diagrams (3 x 5p each = 15p)

**Complete the timing diagram for the specified flip-flops where Qa, Qb, and Qd are the outputs of the D flip-flops, T flip-flops, and JK flip-flops respectively. Assume that the input signal can change only on vertical lines. Ignore the setup time  $t_{su}$  and the hold time  $t_h$  requirements.**

 
- (a) Complete the following timing diagrams for the D input to a Negative edge triggered D flip-flops. Assume the initial value of  $Q_a$  is zero



 - (b) Complete the following timing diagrams for the T input to a positive edge triggered T flip-flops. Assume the initial value of  $Q_b$  is zero



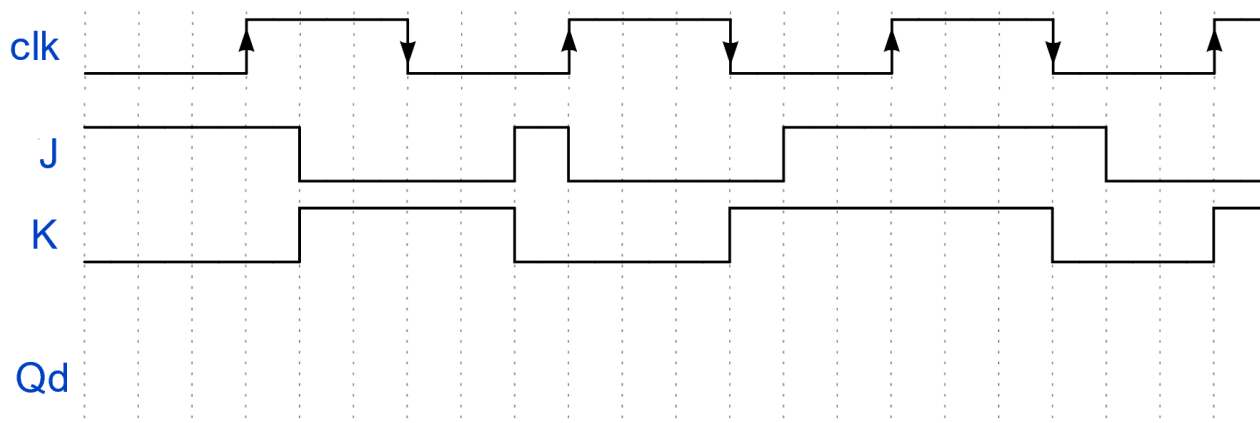- (c) Complete the following timing diagrams for the J and K input to a positive edge triggered JK flip-flops. Assume the initial value of  $Q_d$  is zero



### 6. Multiplexers (15p)

For the following logic function, use Shannon's expansion to derive an implementation using only 2-to-1 multiplexers, and no other logic gates. Assume that the signals A, B, C, and D are available only in their non-inverted form as well as the constants 0 and 1. Clearly label all the inputs, outputs, and pins.

$$Z(A,B,C,D) = \overline{B}\overline{C} + \overline{B}\overline{D} + \overline{C}\overline{D} + A\overline{B} + \overline{A}BCD$$


## 7. Full adder with decoder (4p + 6p = 10p)

- (a) Fill out the truth tables for a full-adder and a 2-4 decoder (using X and Y as the decoder inputs).

X	Y	$C_{in}$	$C_{out}$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$w_1$ (X)	$w_0$ (Y)	$y_3$	$y_2$	$y_1$	$y_0$
0	0				
0	1				
1	0				
1	1				

 - (b) Implement the full-adder using a 2-4 decoder and additional NOT, OR, and AND gates. (Hint: It may help to derive expressions for  $C_{out}$  and S in terms of  $y_3$ ,  $y_2$ ,  $y_1$ , and  $y_0$ ). Two inputs are already assigned.



**8. More Multiplexers (4p + 6p = 10p)**

**Consider the following logic function:  $F = ABC + ABD + A\bar{B}C + A\bar{B}\bar{C}D + BCD$**

(a) Draw the complete truth table

(b) Implement the function **F** using only 4-to-1 MUXs and no other logic gates.



### 9. Comparator (7p + 8p = 15p)

Design a logic circuit that accept 4-bit unsigned binary number as an input, and produces output F=1 when the input number is divisible either by 3 only or 7 only, but not both. The logic circuit must produce output F=0 for all other cases. Assume that the input signals are available in non-inverted/inverted forms as well as the constants 0 and 1. Clearly label all inputs, outputs and pins.

- (a) Draw and complete the truth table for the logic circuit.
- (b) Implement the function using a Decoder and a minimal number of AND, OR, and NOT gates.

<b>Question</b>	<b>Max</b>	<b>Score</b>
1. True/False	10	
2. Logic circuits	20	
3. Addition/Subtraction	15	
4. Number Conversions	20	
5. Timing Diagrams	15	
6. Multiplexers	15	
7. Full-Adder with Decoder	10	
8. More Multiplexer	10	
9. Comparator	15	
<b>TOTAL</b>	<b>130</b>	